

Flexible and Stackable Non-Volatile Resistive Memory for High Integration

Jinho Bae

Ocean System Engineering






Resistive memory: Crossbar array



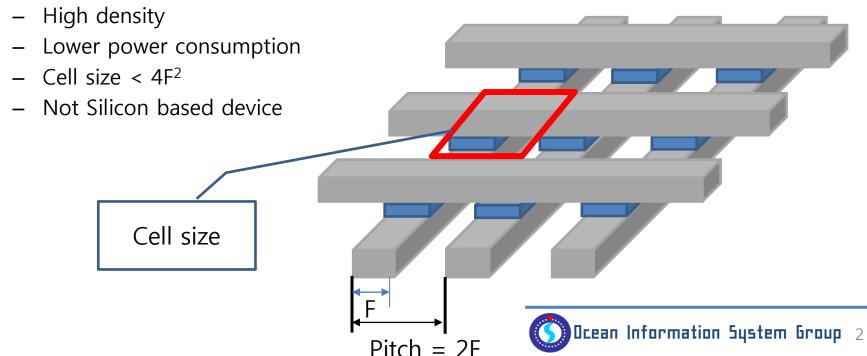- Scaling limitation of the CMOS technology:
 - 2008 International Technology Roadmap for Semiconductors: "Beyond CMOS" → "New switches"
 - N.Z. Haron, S. Hamdioui, Why is CMOS scaling coming to an END?, Design and Test Workshop, IDT 3rd International, 2008 pp. 98-103.






Resistive memory: Sneak current problem



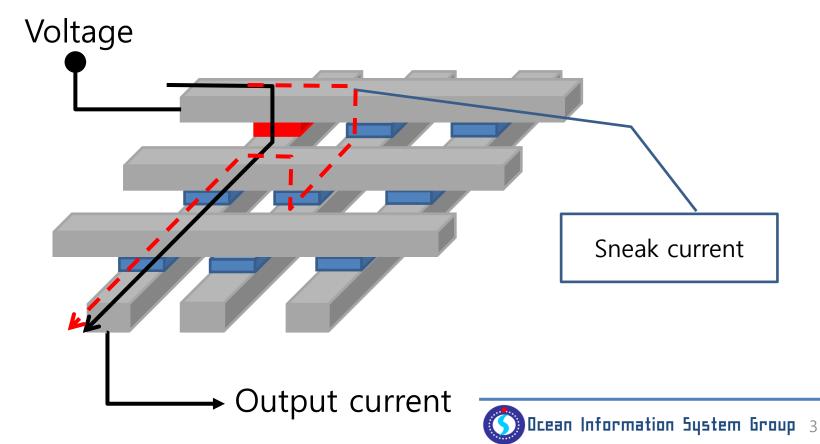Sneak current: make big problems in terms of the data reading/ writing errors and an extra power consumption in read and write Linn, E.; Rosezin, R.; Kugeler, C.; Waser, R. Nat. Mater. 2010, 9, 403-406.




Memristor:



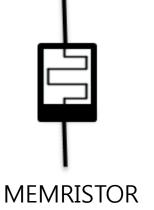Element was proposed by Leon Chua (UC Berkeley) in 1971.






 $d\varphi = M dq$

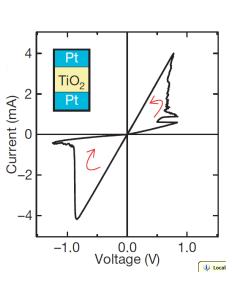R. Stanley Williams (HP Laboratories) found the Memristor in D. B. Strukov, et al., vol 453, 1 May 2008, doi:10.1038/nature06932.






The goal



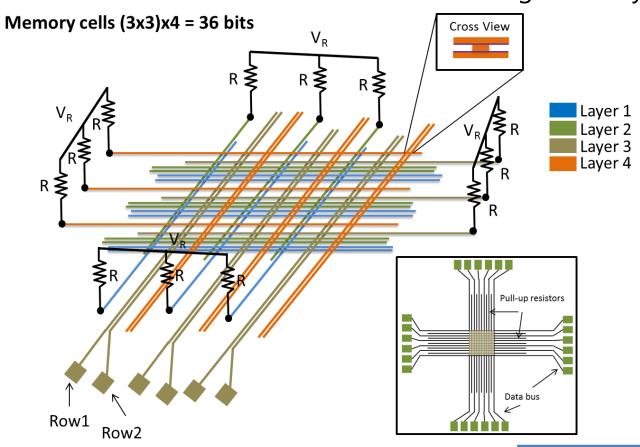
We propose a novel flexible and stackable resistive random access memory (ReRAM) array with multi-layered crossbar structures fabricated on a PET flexible substrate through EHD system.



How to read and write data



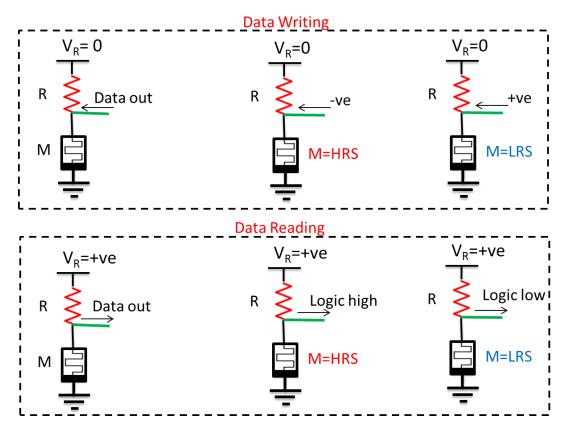Voltage division principal to read/write data:




Writing logic "0" Writing logic "1" Data i/o [V] 2V-0V -2V-0.50. $\sum_{0.25}^{0.50}$ Data i/o [V] Memristor in HR\$ Memristor in LRS Reading logic "1" Reading logic "0" time


Ali, S., Bae, J., Choi, K. H., Lee, C. H., Doh, Y. H., Shin, S., and Kobayashi, N. P., "Organic non-volatile memory cell based on resistive elements through electro-hydrodynamic technique," Organic Electronics 17, 121-128 (2015).

Basic memory cell



Our basic memory cell and operation:

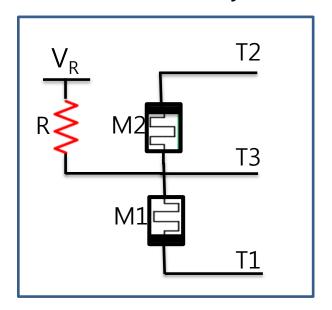

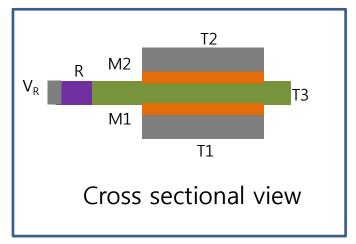

M1 operation

Operation	T ₁	T2	Т3
Write "0"	Groun d	Open	2
Write "1"	Groun d	Open	-2
Read logic 0/1	Groun d	0=0.1V 1=0.9V	1V


M2 operation

Operation	T ₁	T2	Т3
Write "0"	Open	Ground	-2
Write "1"	Open	Ground	2
Read logic 0/1	Groun d	0=0.1V 1=0.9V	1V

Fabrication




Deposition layer and crossbar:

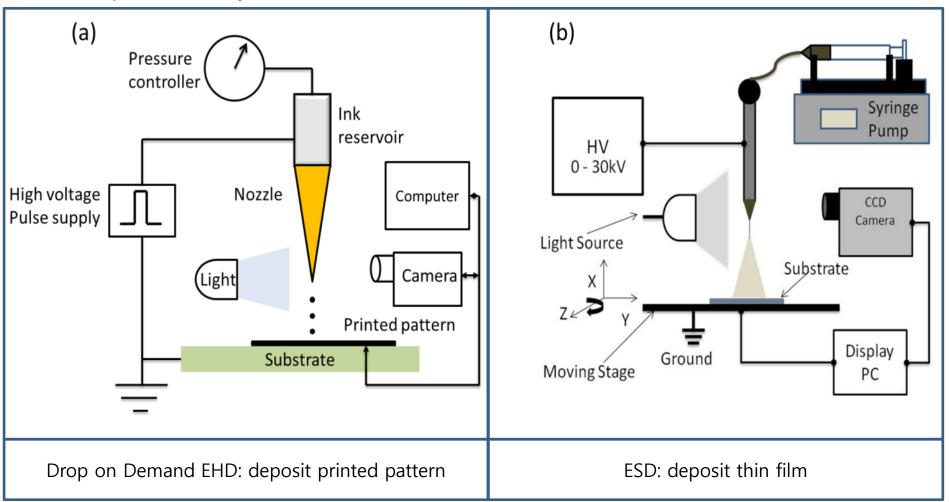

Memristor



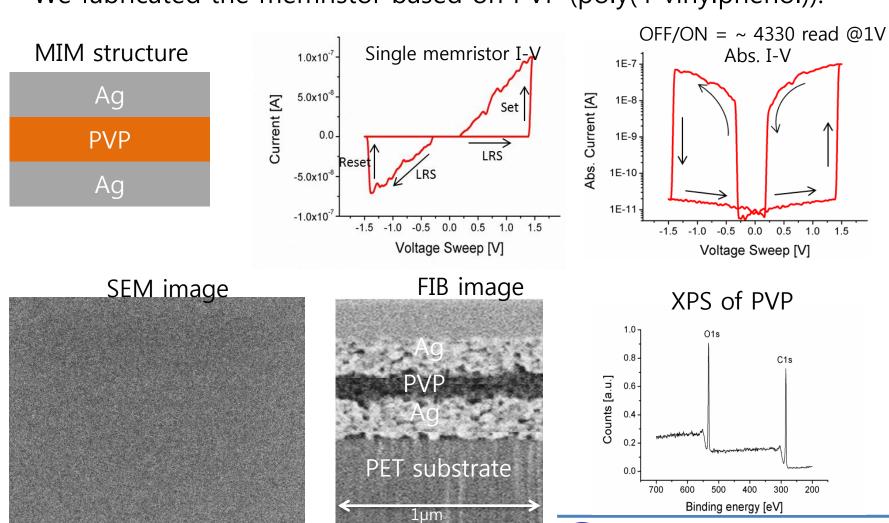We fabricated the memristor based on PVP (poly(4-vinylphenol)):





HRS: 66.66 G Ω , LRS: 14.28 G Ω

Pull-up resistor



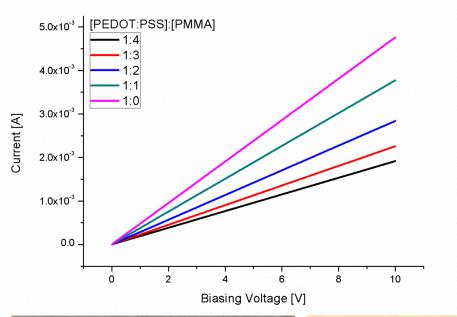• Pull-up resistor based on MEH:PPV and PMMA: 20 M Ω



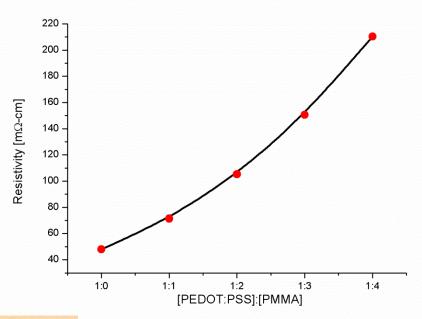






Ali, S., Bae, J., and Lee, C. H., "Design of versatile printed organic resistor based on resistivity (ρ) Control," Appl. Phys. A 119, 1499-1506 (2015).

Fabricated two layered 3×3 memory




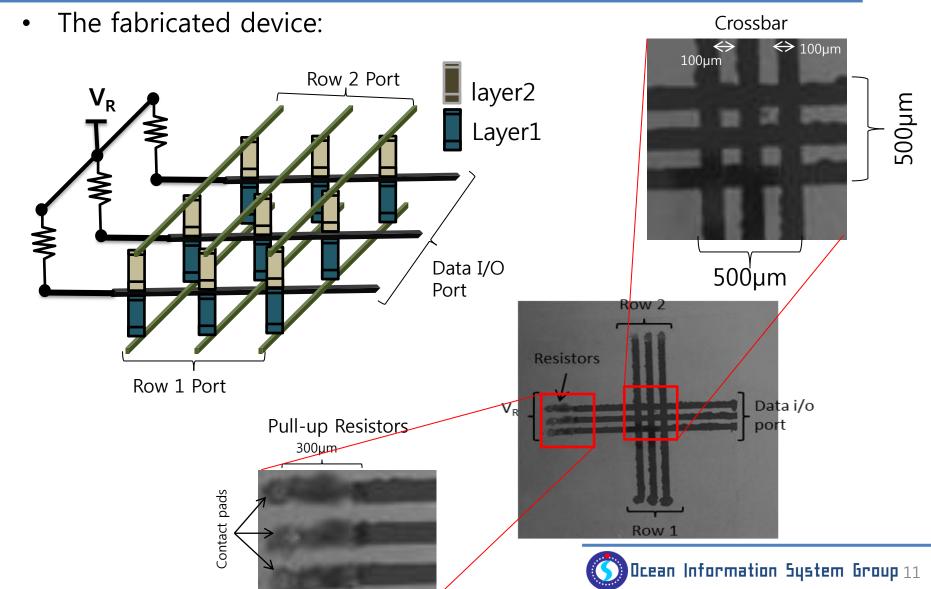


Read data



The fabricated device:

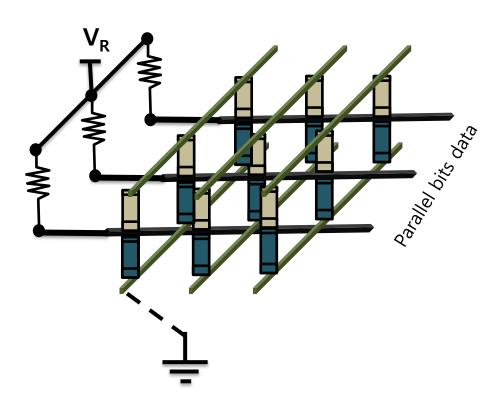

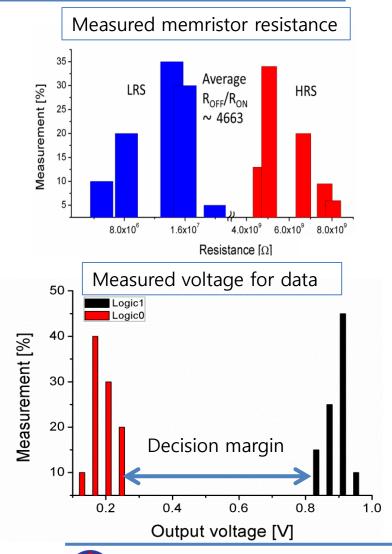
It has a higher decision margin, but it has a problem In occasions of a worst case by sneak current.



Reading problem with sneak current



• Memory circuit with sneak current:

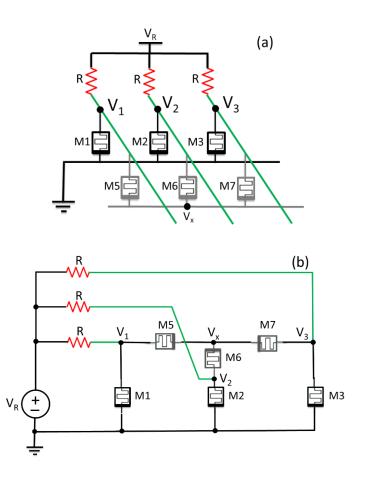



(a) A 2×3 memory array during data reading cycle. (b) Equivalent resistive circuit.

Writing problem with sneak current



Memory circuit with sneak current:

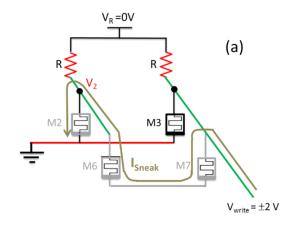

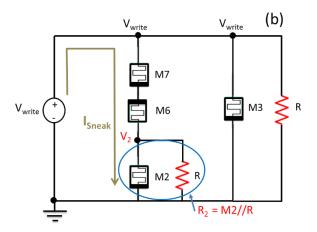

If
$$V_2 = \frac{R_2 V_{write}}{M6 + M7 + R_2}$$
 > |Voltage of state switch|,

M2 is changed by the sneak current.

However, the proposed circuit avoid this problem Due to $|V_2|$ < |Voltage of state switch|.

Here, R_2 is sufficiently decreased by R because R Is smaller than M.

a) A 2×2 memory array during data writing cycle of the proposed structure. (b) Equivalent resistive circuit.



Conclusions



- We have proposed stackable memory based on materials PVP for memristor and MEH:PPV and PMMA for pull up resistor through EHD technology.
- We have fabricated two layered 3×3 memory.
- The resistance of the fabricated memristor is about HRS = 66.66 G Ω and LRS = 14.28 G Ω .
- The resistance of the fabricated memristor is 20 M Ω .
- The proposed device was obtained zero detection error, experimentally.
- The sneak current problem:
 - Read cycle: occurred several problem, but we can reduced this problem by choosing resistances of memristors and pull up resistors.
 - Write cycle: avoid the problem by the pull up resistors.

Thank you for your attention!



